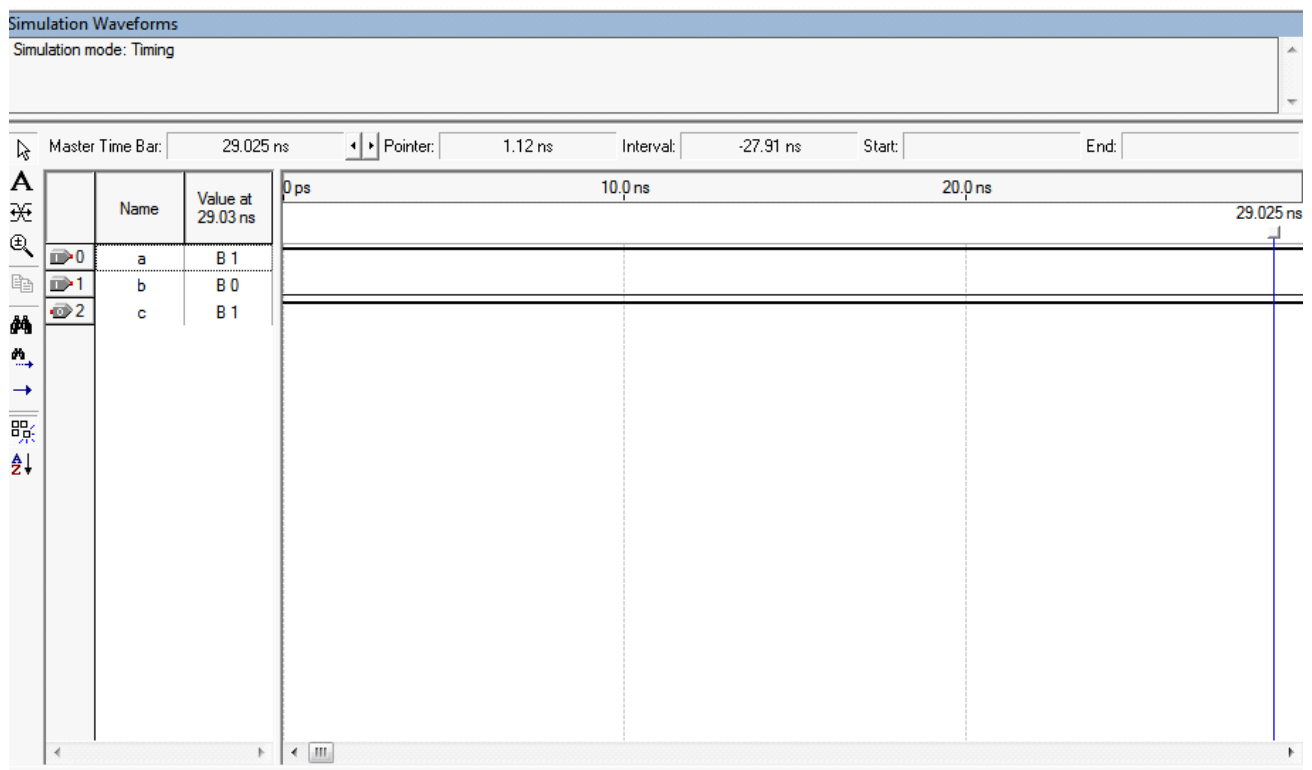


EX NO: 18


1.OR GATE

```
module or1 (c,a,b);  
    output c;  
    input a,b;  
    assign c=a|b;  
endmodule
```

Simulation:




RTL view:

 


2.AND GATE

```
module and1(c,a,b);  
  output c;  
  input a,b;  
  assign c=a&b;  
endmodule
```

Simulation:

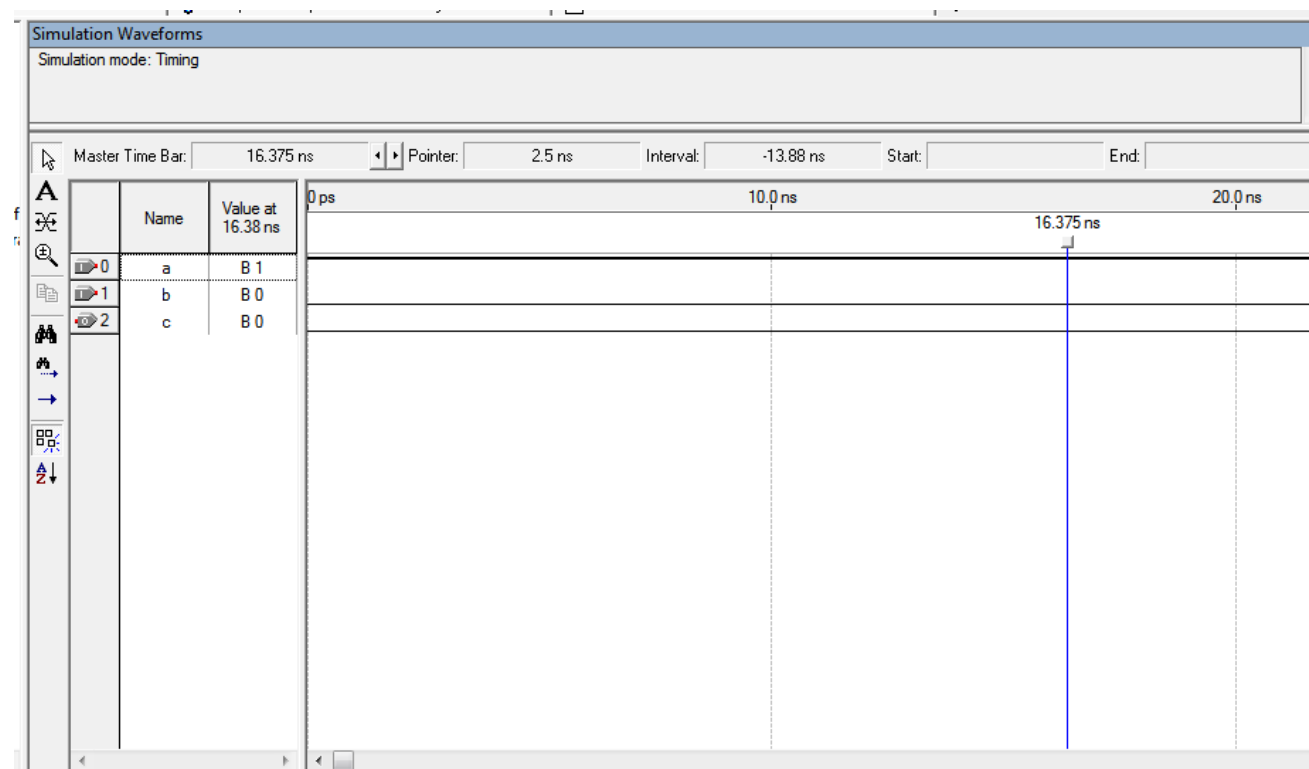



RTL view:

 

3.NOT GATE

```
module inv(o,a);  
  output o;  
  input a;  
  assign o=~a;  
endmodule
```


Simulation:

 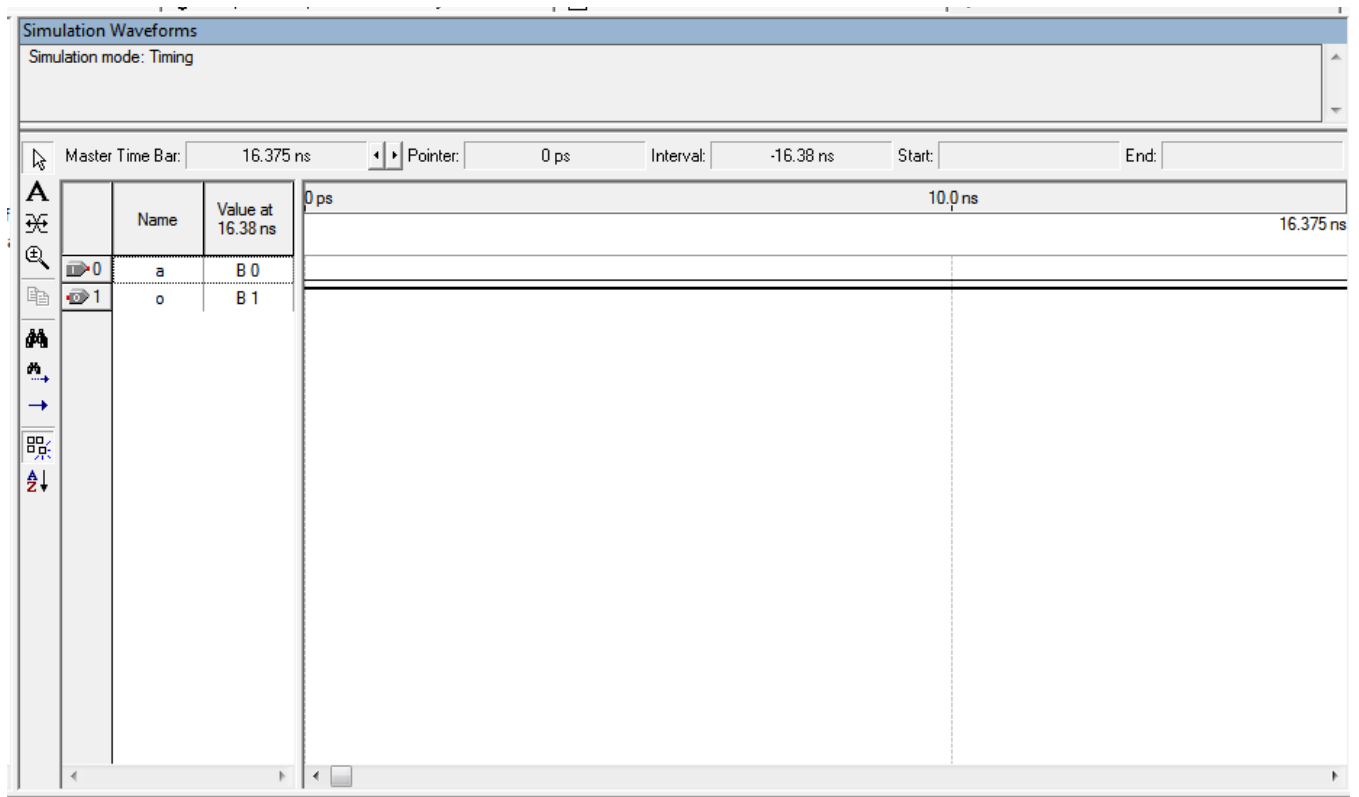


4. NOR GATE

```
module nor1(c,a,b);
    output c;
    input a,b;
    wire d;
    or1 u1(d,a,b);
    inv u2(c,d);
endmodule
module or1(c,a,b);
    output c;
    input a,b;
    assign c=a|b;
endmodule
module inv(o,a);
    output o;
    input a;
    assign o=~a;
endmodule
```

Simulation:

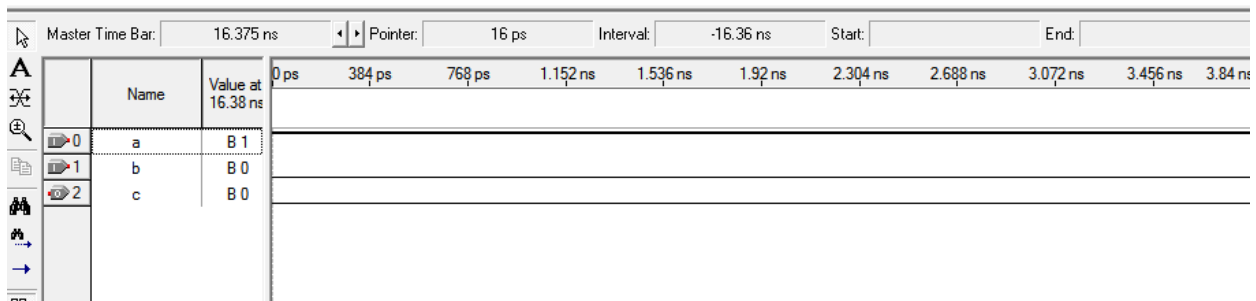

RTL view:

 


5.NAND GATE

```
module nand1(c,a,b);  
    output c;  
    input a,b;  
    wire d;  
    and1 u1(d,a,b);  
    inv u2(c,d);  
endmodule  
module and1(c,a,b);  
    output c;  
    input a,b;  
    assign c=a&b;  
endmodule  
module inv(o,a);  
    output o;  
    input a;  
    assign o=~a;  
endmodule
```

Simulation:



RTL view:

 

6.EX OR GATE

exor

```
module exor1(c,a,b);
```

```
input a;
```


```
input b;
```

```
output c;
```


```
assign c=(a&~b)|(~a&b);
```

```
endmodule
```

Simulation:

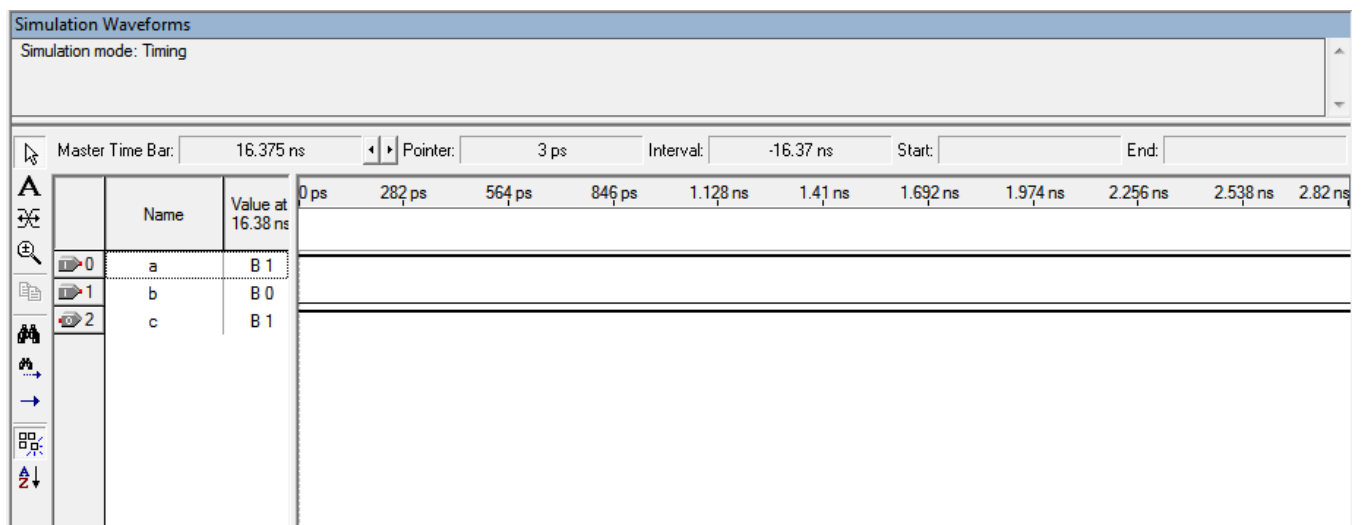


RTL view:

 


7.EX NOR GATE

```
module exnor1(c,a,b);  
input a;  
input b;  
output c;  
assign c=~((a&~b)|(~a&b));  
endmodule
```

Simulation:

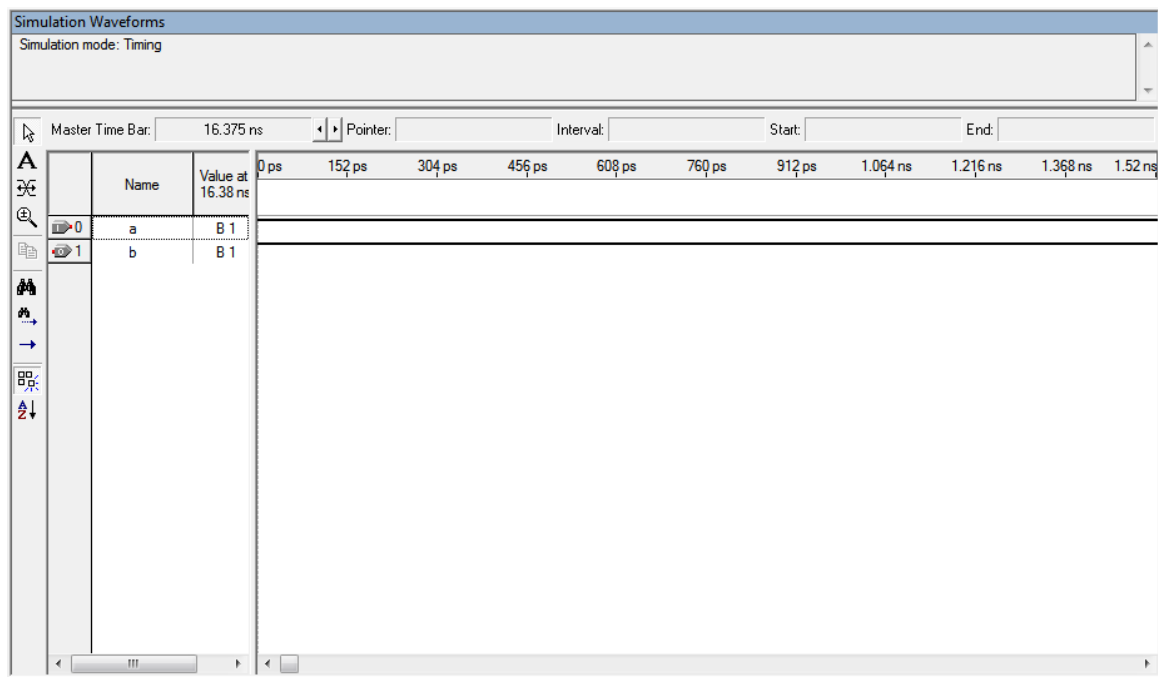

RTL view:

 


8.BUFFER

```
module buffer1(o,a);  
output o;  
input a;  
assign o=~(~(a));  
endmodule
```

Simulation:

	Name	Value at 25.73 ns	0 ps	8 ps	16 ps	24 ps	32 ps	40 ps	48 ps	56 ps	64 ps	72 ps	80 ps	88 ps
0	a	B 1												
1	o	B 1												

RTL View:

 


EX NO: 19


1.HALF ADDER

```
module half_adder(in_x, in_y, out_sum, out_carry);  
input in_x;  
input in_y;  
output out_sum;  
output out_carry;  
assign out_sum = in_x^in_y;  
assign out_carry = in_x&in_y;  
endmodule
```

Simulation:

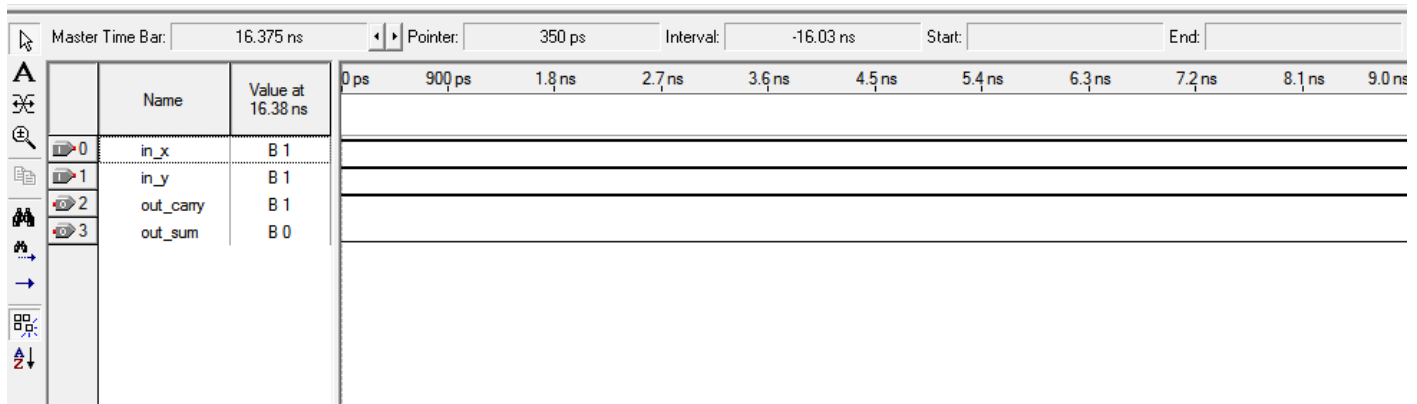


RTL view:

 


2.FULL ADDER

```
module fulladder(  
    input a,  
    input b,  
    input cin,  
    output sum,  
    output carry );  
    assign x=a ^ b;  
    assign sum=x^cin;  
    assign y=x & cin;  
    assign z=a & b;  
    assign carry= y | z;  
endmodule
```

Simulation:

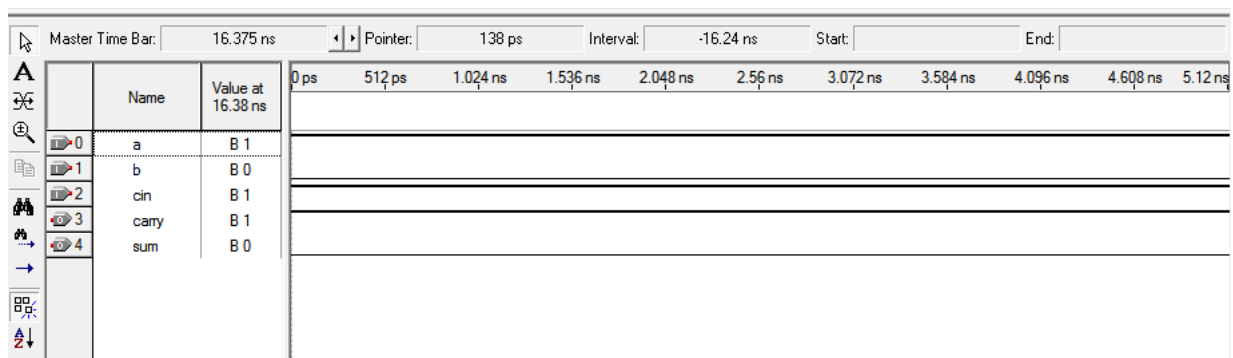

RTL view:

 

3. 4-BIT MAGNITUDE COMPARATOR

```
module comparator(a,b,eq,lt,gt);
```

```
input [3:0] a,b;
```

```
output reg eq,lt,gt;
```

```
always @(a,b)
```

```
begin
```

```
if (a==b)
```

```
begin
```

```
eq = 1'b1;
```

```
lt = 1'b0;
```

```
gt = 1'b0;
```

```
end
```

```
else if (a>b)
```

```
begin
```

```
eq = 1'b0;
```

```
lt = 1'b0;
```

```
gt = 1'b1;
```

```
end
```

```
else
```

```
begin
```

```
eq = 1'b0;
```

```
lt = 1'b1;
```


```
gt = 1'b0;
```

```
end
```


```
end
```

```
endmodule
```

Simulation:

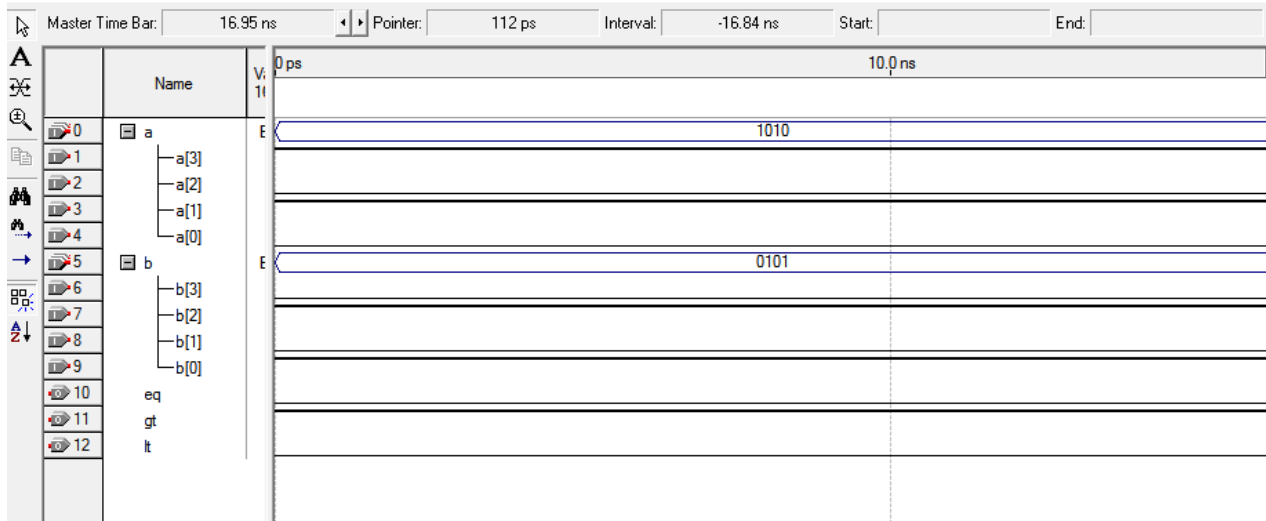


RTL view:

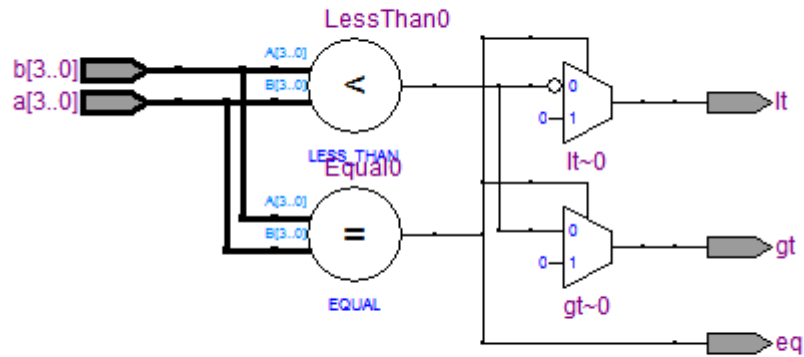


4. 2:4 DECODER

```
module dec2_4(a,b,en,y0,y1,y2,y3);  
input a,b,en;  
output y0,y1,y2,y3;  
assign y0= (~a) & (~b) & en;  
assign y1= (~a) & b & en;  
assign y2= a & (~b) & en;  
assign y3= a & b & en;  
endmodule
```

Simulation:

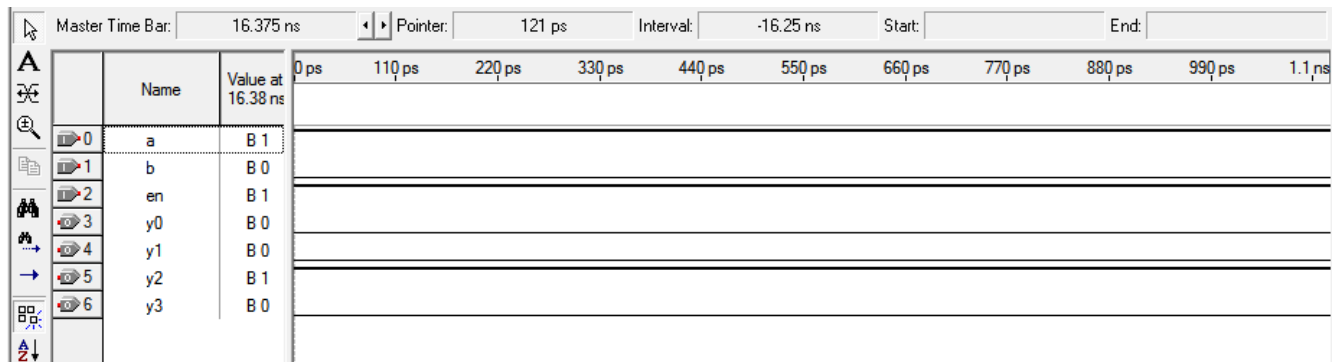

RTL view:

 

5. 4:2 ENCODER

```
module encoder4_2 ( a ,b ,c ,d ,x ,y );
```

```
output x ;
```

```
output y ;
```

```
input a ;
```

```
input b ;
```

```
input c ;
```


```
input d ;
```

```
assign x = b | d;
```


```
assign y = c | d;
```

```
endmodule
```

Simulation:

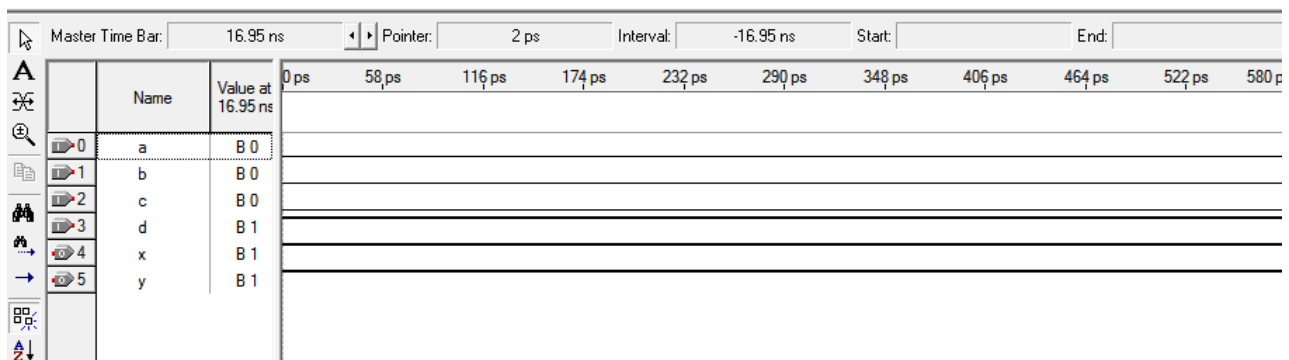


RTL view:

 


6. 4:1 MUX

```
module mux4to1 ( input [3:0] a, // 4-bit input called a
  input [3:0] b, // 4-bit input called b
  input [3:0] c, // 4-bit input called c
  input [3:0] d, // 4-bit input called d
  input [1:0] sel, // input sel used to select between a,b,c,d
  output reg [3:0] out); // 4-bit output based on input sel
// This always block gets executed whenever a/b/c/d/sel changes value
// When that happens, based on value in sel, output is assigned to either a/b/c/d
always @ (a or b or c or d or sel) begin
  case (sel)
    2'b00 : out <= a;
    2'b01 : out <= b;
    2'b10 : out <= c;
    2'b11 : out <= d;
  endcase
end
endmodule
```

Simulation:

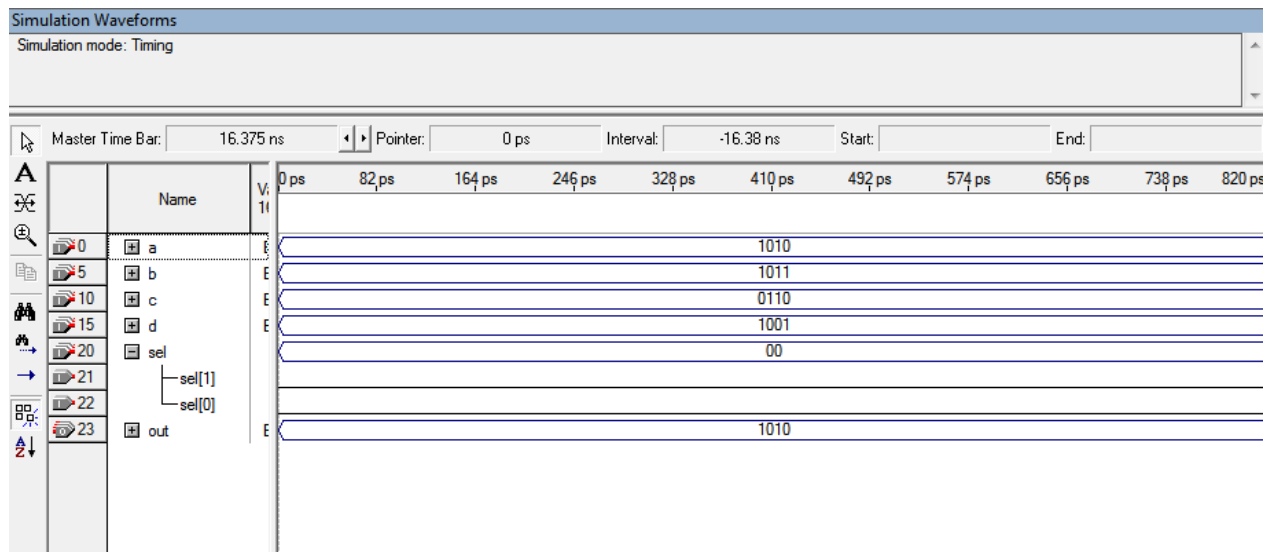


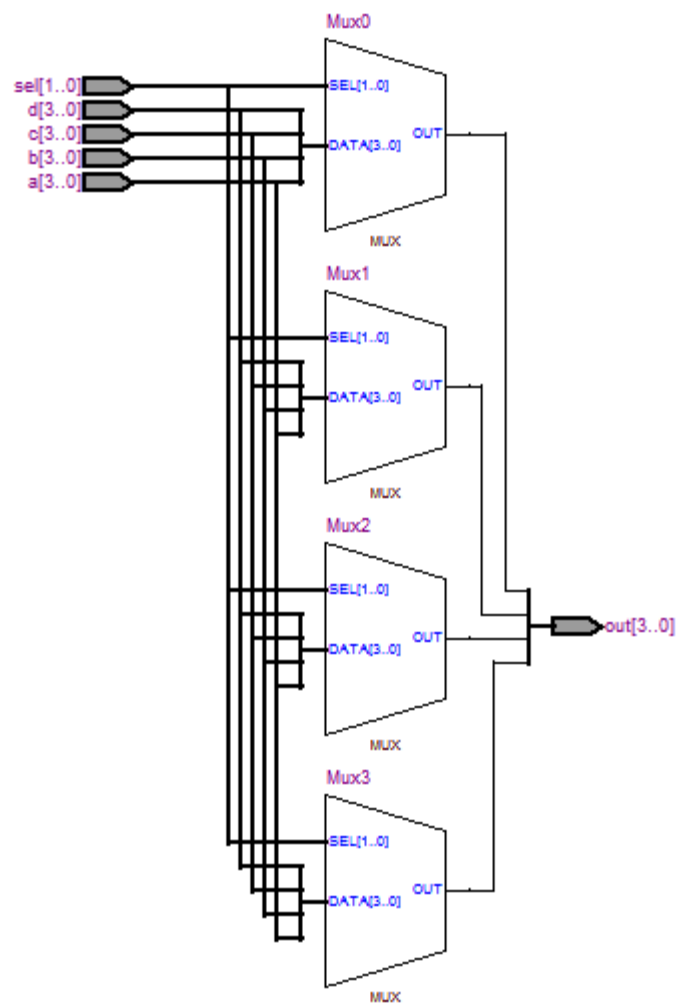


7. 1:4 DEMUX

```
module demux1_4 ( din ,x ,y ,a ,b ,c ,d );  
output a ;  
output b ;  
output c ;  
output d ;  
  
input din ;  
input x ;  
input y ;  
  
assign a = din & (~x) & (~y);  
assign b = din & (~x) & y;  
assign c = din & x & (~y);  
assign d = din & x & y;  
endmodule
```

Simulation:

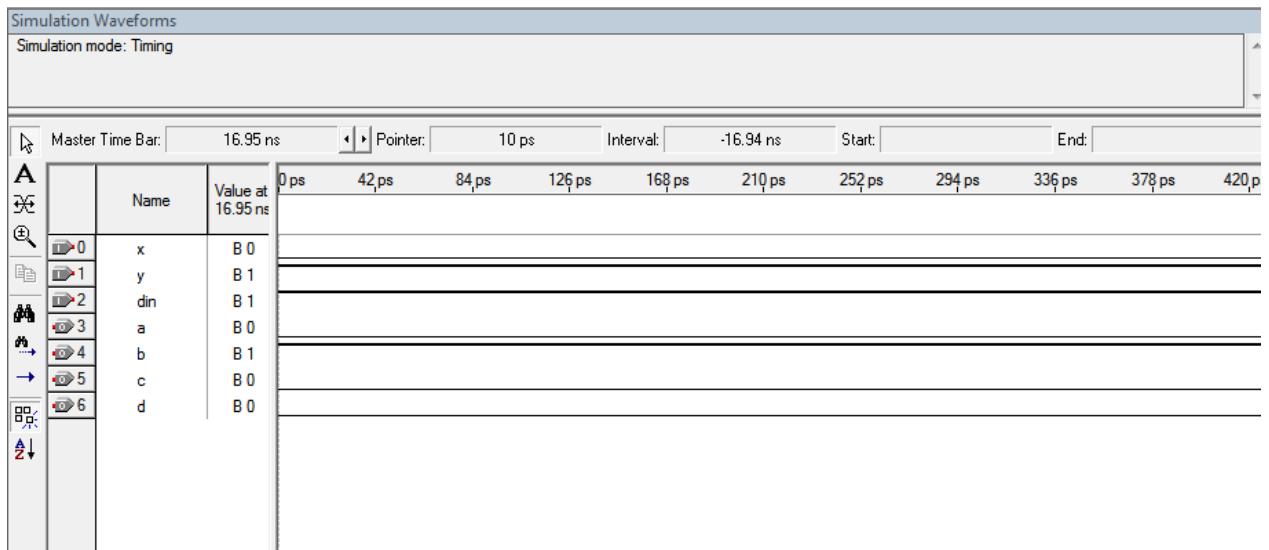

RTL view:

 


EX NO: 20


1.D FLIP DLOP

```
module d(q,q1,d,c);
output q,q1;
input d,c;
reg q,q1;
initial
begin
    q=1'b0; q1=1'b1;
end
always @ (posedge c)
begin
    q=d;
    q1= ~d;
end
endmodule
```

Simulation:

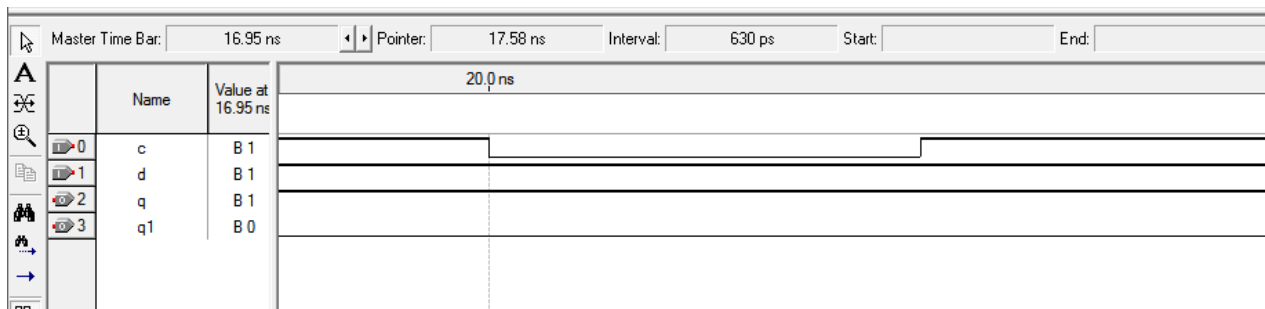


RTL view:

 


2. JK FLIP FLOP

```
module jk(q,q1,j,k,c);
output q,q1;
input j,k,c;
reg q,q1;
initial begin q=1'b0; q1=1'b1; end
always @ (posedge c)
begin
    case({j,k})
        {1'b0,1'b0}:begin q=q; q1=q1; end
        {1'b0,1'b1}: begin q=1'b0; q1=1'b1; end
        {1'b1,1'b0}:begin q=1'b1; q1=1'b0; end
        {1'b1,1'b1}: begin q=~q; q1=~q1; end
    endcase
end
endmodule
```

Simulation:

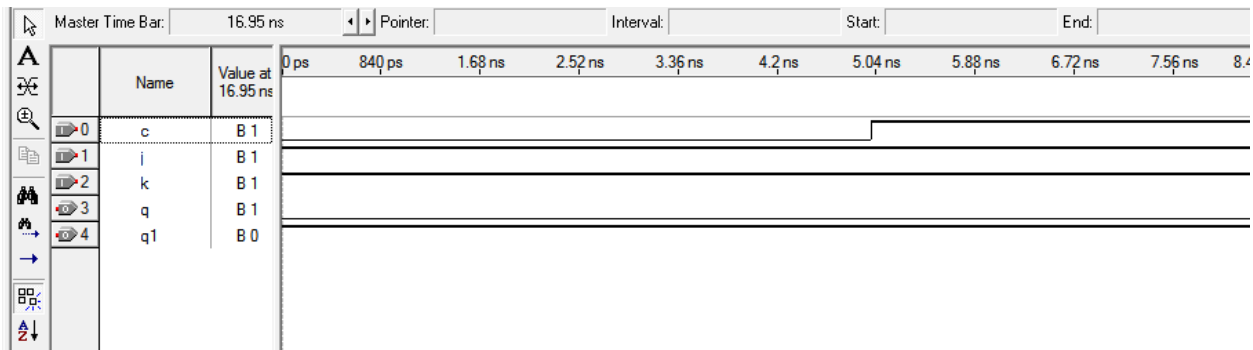

RTL view:

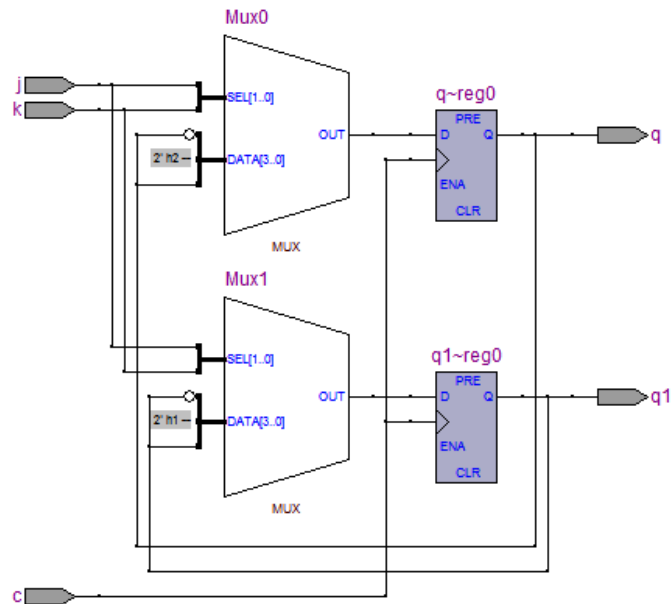


3. T Flip Flop


```
module TFlipFlop1(q,q1,t,c);
output q,q1;
input t,c;
reg q,q1;

initial
begin
    q=1'b0; q1=1'b1;
end
always @ (posedge c)
begin
    q = (t&(~q))|((~t)&q);
    q1= ~q;
end
endmodule
```

Simulation:

 


RTL View:

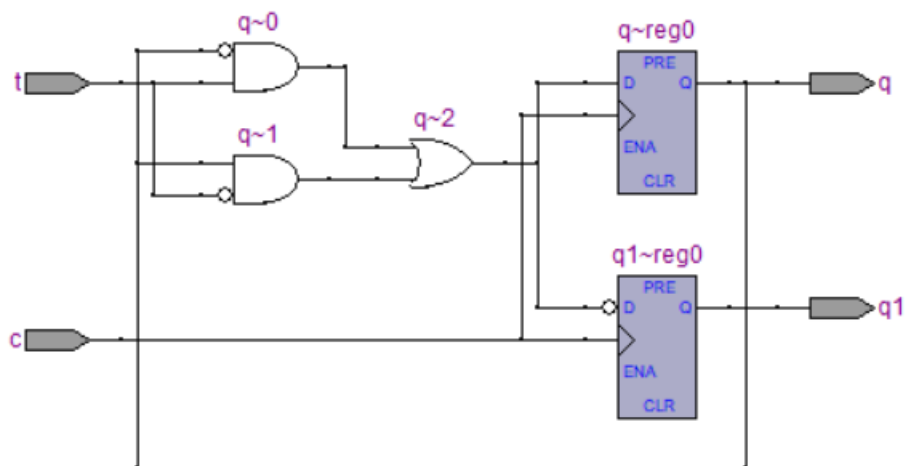


4. SR Flip Flop

```
module SRFlipFlop1(q,q1,s,r,c);
output q,q1;
input s,r,c;
reg q,q1;
initial
    begin
        q=1'b0; q1=1'b1;
    end
always @ (posedge c)
    begin
        q = s | ((~r) & q);
        q1= ~q;
    end
endmodule
```

Simulation:

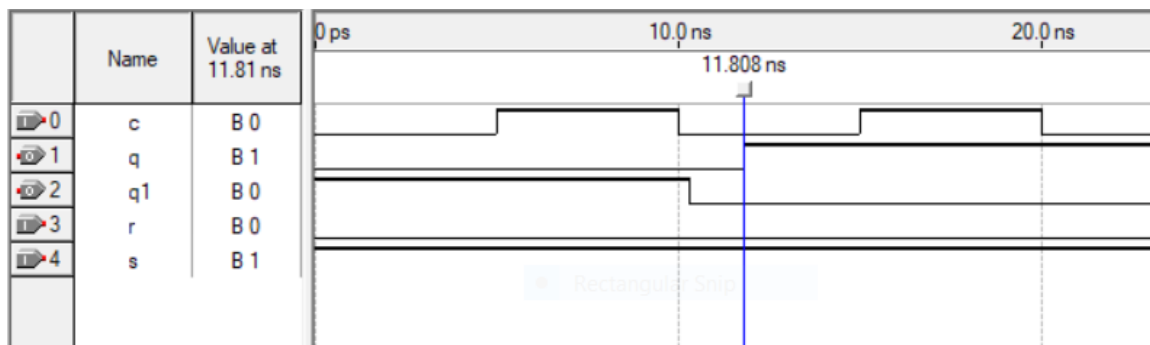


RTL View:

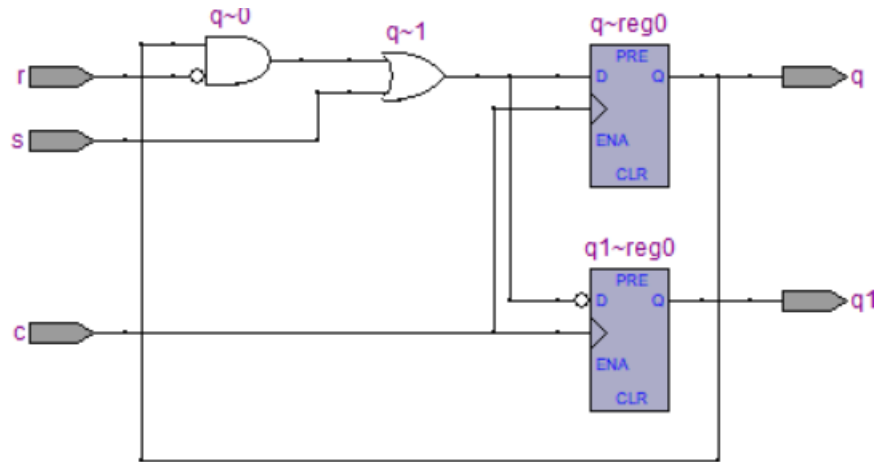


5. 4 Bit Shift Register [SIPO]

```
module sipo(sout,s1out,sin,clk);
output [3:0]sout,s1out;
input sin,clk;
d u1(sout[0],s1out[0],sin,clk);
d u2(sout[1],s1out[1],sout[0],clk);
d u3(sout[2],s1out[2],sout[1],clk);
d u4(sout[3],s1out[3],sout[2],clk);
endmodule
module d(q,q1,d,c);
output q,q1;
input d,c;
reg q,q1;
initial
begin
q=1'b0; q1=1'b1;
end
always @ (posedge c)
begin
q=d;
q1= ~d;
end
endmodule
```


Simulation:

 


RTL View:

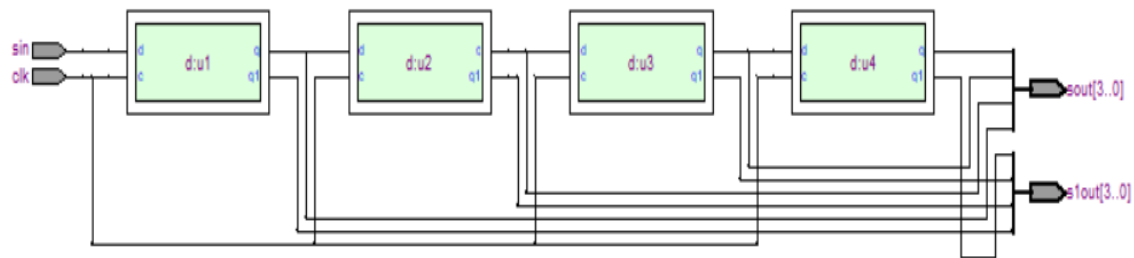


6. 4 Bit Up Counter

```
module UpCounter(clk, reset, Q);
input clk, reset;
output [3:0] Q;
reg [3:0] Q;
always @ (posedge clk)
begin
    if (~reset)
        begin
            Q <= Q+1;
        end
    else
        Q=0;
end
endmodule
```

Simulation:

 

RTL View:

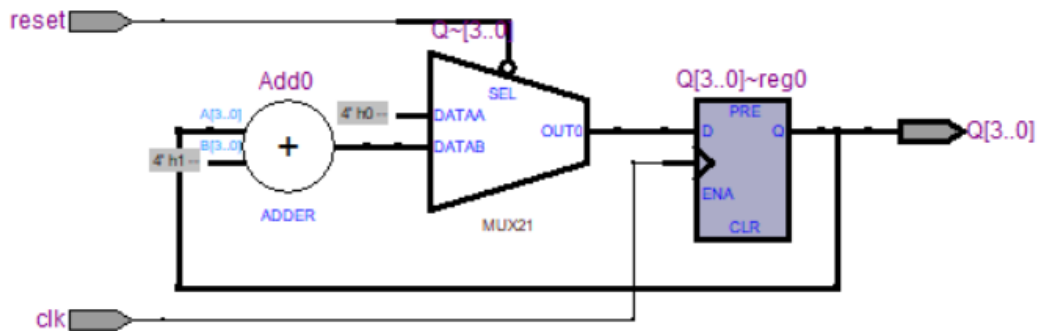


7. 4 Bit Down Counter:

```
module DownCounter(clk, reset, Q);  
input clk, reset;  
output [3:0] Q;  
reg [3:0] Q;  
always @ (posedge clk)
```

```
begin  
    if (~reset)  
        begin  
            Q <= Q-1;  
        end  
    else  
        Q <= 15;  
    end  
end  
endmodule
```

Simulation:

 

RTL View:

